

# STEP FPGA drives the nixie tube module based on 74HC595


In this section, we will use the 6-digit digital tube on the FPGA driver board to realize dynamic display.

## ====Hardware description====

In the introductory tutorial before in front of the digital display separate chapter has introduced the LED independent display relevant content for everyone, on a separate display will not repeat here. There are 6-digit digital tubes on our bottom board. According to the different driving methods, there are the following comparisons:

**Independent display:** to control each digital tube requires at least 8 I/O ports to control, 6-digit digital tubes need  $6 \times 8 = 48$  signals. The lines can be displayed separately. The independent display is simple to implement, but requires a lot of signal lines.


**Scanning display:** Connect the same segment selection signal of each digital tube together, so we only need 8 segment selection signals and 6 position selection signals, a total of 14 signals. Scanning display can effectively save I/O port resources, which is slightly more complicated to implement. The 6-digit common cathode digital tube used on the bottom board of our little foot, the principle of analysis and scanning display is as follows: At a certain moment, FPGA controls 8 common segment selection interfaces to output the digital tube font data 8'h06 (DP=0, G=0, F=0, E=0, D=0, C=1, B=1, A=0), the 6-digit digital tube is controlled at the same time only the first bit is enabled (DIG1=0, DIG2=1, DIG3=1, DIG4=1, DIG5=1, DIG6=1). In this way, we will see that the first digital tube displays the number 1, and the other 5 digital tubes do not display. If you don't understand, you can refer to the experiment in the introductory tutorial IV: LED independent display section according to the scanning manner, divided into a total of 6 time segments corresponding to selected output ports are six digital font data to be displayed, each time the bit selected from the port remains only an LED is enabled. State, 6 moments in turn, when the scanning frequency is high enough (for example, when the scanning frequency is equal to 100Hz), the display of the digital tube seen by the human eye is continuous, and what we see is 6 different numbers.

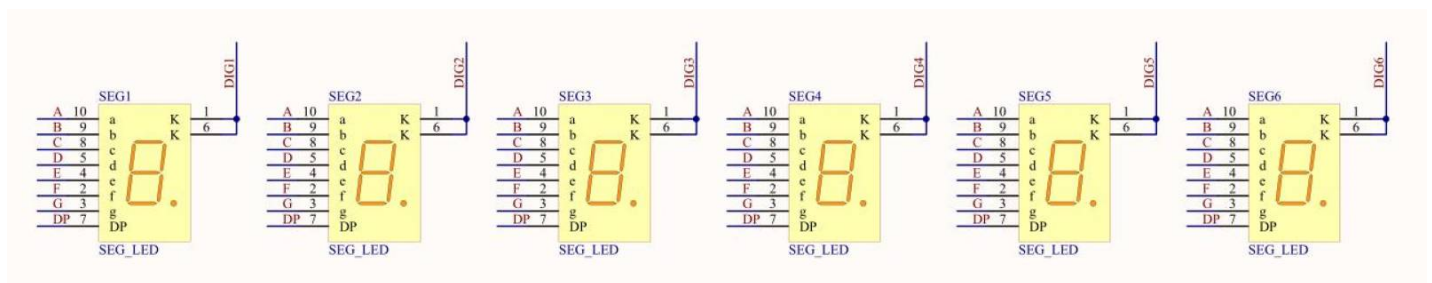


The above has introduced two methods of independent display and scanning display of the digital tube. The scanning display method uses 14 I/O ports to control. Compared with a simple processor, 14 I/O ports are also very much. Here we use a common driver chip 74HC595, let's take a look:

74HC595 is a more commonly used serial to parallel chip, which integrates an 8-bit shift register, a memory and 8 three-state buffer outputs. In the simplest case, we only need to control 3 pin inputs to get 8 pin parallel output signals, and it can be used in cascade. We use 3 I/O ports to control two cascaded 74HC595 chips to generate 16 channels Parallel output, connected to the 6-digit digital tube scanning display, can easily complete the digital tube driving task. Different IC manufacturers can produce 74HC595 chips with the same functions. However, the chip manuals of different



manufacturers have different pin names. The pin order is the same. You can identify the hardware of the 74HC595 chip in this design. For circuit connection, refer to the 74HC595 data manual for its specific usage. In the figure below, we understand that the OE# (G#) and MR# (SCLR#) signals are output enable (low-level output) and reset pins (low-level complex Bit), OE# (G#) we connect GND to enable the chip output, MR# (SCLR#) we connect VCC so that the shift register of the chip will never be reset, so FPGA only needs to control SH CP (SCK), ST CP (RCK) and DS (SER).

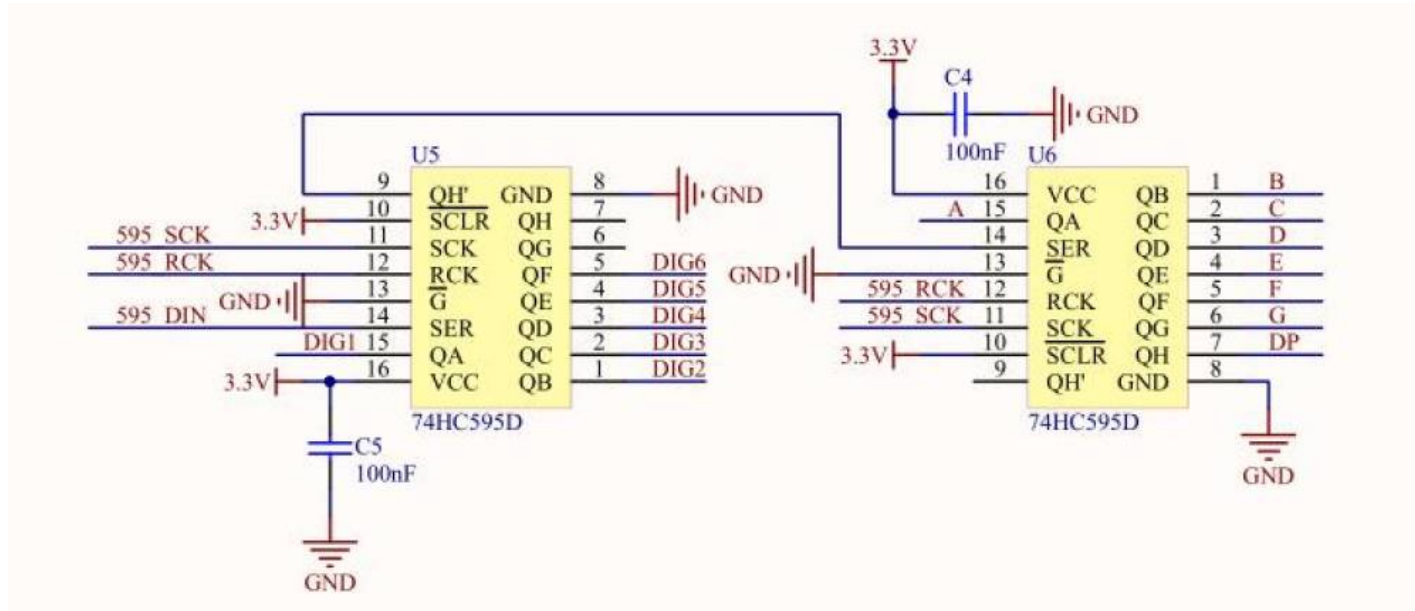

INPUT					OUTPUT		FUNCTION
SH_CP	ST_CP	OE	MR	DS	Q7'	Qn	
X	X	L	L	X	L	n.c.	a LOW level on MR only affects the shift registers
X	↑	L	L	X	L	L	empty shift register loaded into storage register
X	X	H	L	X	L	Z	shift register clear; parallel outputs in high-impedance OFF-state
↑	X	L	H	H	Q6'	n.c.	logic high level shifted into shift register stage 0; contents of all shift register stages shifted through, e.g. previous state of stage 6 (internal Q6') appears on the serial output (Q7')
X	↑	L	H	X	n.c.	Qn'	contents of shift register stages (internal Qn') are transferred to the storage register and parallel output stages
↑	↑	L	H	X	Q6'	Qn'	contents of shift register shifted through; previous contents of the shift register is transferred to the storage register and the parallel output stages

 

MLA010

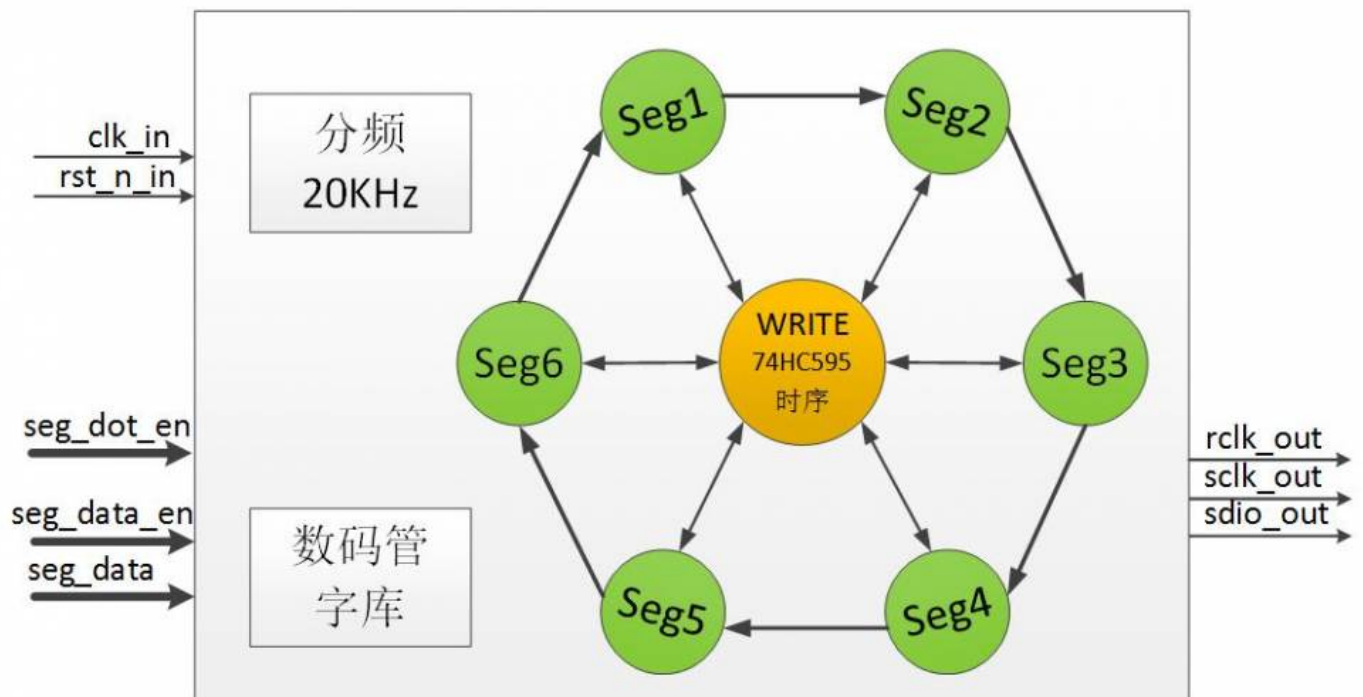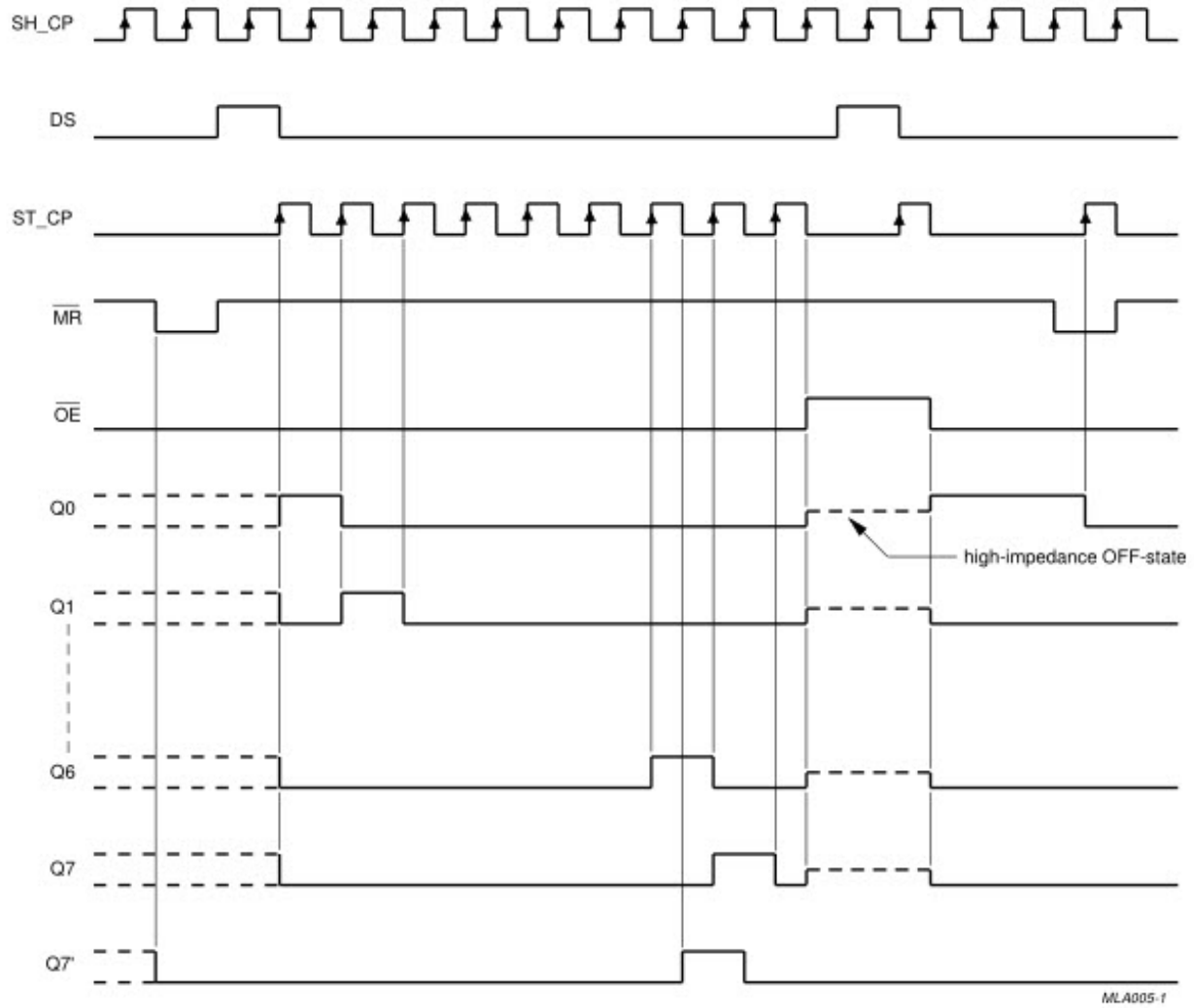

# ====Verilog code=====

---

6/11

```

seg [ 2 ] = 8'h5b ; // 2
seg [ 3 ] = 8'h4f ; // 3
seg [ 4 ] = 8'h66 ; // 4
seg [ 5 ] = 8'h6d ; // 5
seg [ 6 ] = 8'h7d ; // 6
seg [ 7 ] = 8'h07 ; // 7
seg [ 8 ] = 8'h7f ; // 8
seg [ 9 ] = 8'h6f ; // 9
seg [ 10 ] = 8'h77 ; // A
seg [ 11 ] = 8'h7c ; // b
seg [ 12 ] = 8'h39 ; // C
seg [ 13 ] = 8'h5e ; // d
seg [ 14 ] = 8'h79 ; // E
seg [ 15 ] = 8'h71 ; // F
end

//The counter counts the system clock signal
reg [ 9 : 0 ] cnt = 0 ;
always @ ( posedge clk_in or negedge rst_n_in ) begin
    if ( ! Rst_n_in ) begin
        cnt <= 1'b0 ;
    end else begin
        if ( cnt >= ( CLK_DIV_PERIOD - 1 ) ) cnt <= 1'b0 ;
        else cnt <= cnt + 1'b1 ;
    end
end

// generates a pulse signal frequency-divided according to the period counted by the counter
REG CLK_DIV ;
Always @ ( posedge CLK_IN or negedge rst_n_in ) the begin
    IF ( ! Rst_n_in ) the begin
        CLK_DIV <= 1'b0 ;
    End the else the begin
        IF ( CNT == ( CLK_DIV_PERIOD - 1 ) ) clk_div <= 1'b1 ;
        else clk_div <= 1'b0 ;
    end
end

//Use the state machine to complete the scanning of the digital tube and the realization of 74
HC595 timing
reg [ 15 : 0 ] data_reg ;
reg [ 2 : 0 ] cnt_main ;
reg [ 5 : 0 ] cnt_write ;
reg [ 2 : 0 ] state = IDLE ;
always @ ( posedge clk_in or negedge rst_n_in ) begin
    if ( ! rst_n_in ) begin //In the reset state, each register is set to the initial value
        state <= IDLE ;
        cnt_main <= 3'd0 ;
        cnt_write <= 6'd0 ;
        sdio_out <= 1'b0 ;
        sclk_out <= LOW ;
        rclk_out <= LOW ;
    end
end

```

```

end else begin
    case ( state )
        IDLE : begin        //IDLE as the first state is equivalent to soft reset
                            state <= MAIN ;
                            cnt_main <= 3'd0 ;
                            cnt_write <= 6'd0;
                            sdio_out <= 1'b0 ;
                            sclk_out <= LOW ;
                            rclk_out <= LOW ;

                            end
        MAIN : begin
            if ( cnt_main >= 3'd5 ) cnt_main <= 1'b0 ;
            else cnt_main <= cnt_main + 1'b1 ;
            case ( cnt_main )
                //Scan the 6-digit digital tube bit by bit
                3'd0 : begin
                    state <= WRITE ;
                    //After configuring the data sent to 74HC595, jump to the WRITE state and complete the serial
                    sequence
                    data_reg <= { seg [ s
eg_data_1 ] | ( seg_dot_en [ 0 ] ? 8'h80 : 8'h00 ) , seg_data_en [ 0 ] ? 8'hfe : 8'hff } ;
                    //data_reg[15:8] is se
                    gment selection, data_reg[7:0] is bit selection
                    //seg[seg_data_1] is t
                    o obtain corresponding font data according to port input
                    //seg_dot_en[0]?8'h8
                    0:8'h00 is to control the level of the decimal point DP segment of the SEG1 digital tube accor
                    ding to the decimal point display enable signal
                    //seg_data_en[0]? 8'hf
                    e:8'hff is to control SEG1 according to the data display enable signal The level of the bit se
                    lection pin of the digital tube

                    end
                3'd1 : begin
                    state<= WRITE ;
                    data_reg <= { seg [ s
eg_data_2 ] | ( seg_dot_en [ 1 ] ? 8'h80 : 8'h00 ) , seg_data_en [ 1 ] ? 8'hfd : 8'hff } ;
                    end
                3'd2 : begin
                    state <= WRITE ;
                    data_reg <= { seg [ s
eg_data_3 ] | ( seg_dot_en [ 2 ] ? 8'h80 : 8'h00 ) , seg_data_en [ 2 ] ? 8'hfb : 8'hff } ;
                    end
                3'd3 : begin
                    state <= WRITE ;
                    data_reg <= { seg [ s
eg_data_4 ] | ( seg_dot_en [ 3 ] ? 8'h80 : 8'h00 ) , seg_data_en [ 3 ] ? 8'hf7 :8'hff } ;
                    end
                3'd4 : begin
                    state <= WRITE ;
                    data_reg <= { seg [ s
eg_data_5 ] | ( seg_dot_en [ 4 ] ? 8'h80 : 8'h00 ) , seg_data_en [ 4 ] ? 8'hef : 8'hff } ;
                    end
                3'd5 : begin

```



```

state <= WRITE ;
data_reg <= { seg [ se
g_data_6 ] | ( seg_dot_en [ 5 ] ? 8'h80 : 8'h00 ) , seg_data_en [ 5 ] ? 8'hdf : 8'hff } ;
end
default : state <= IDLE ;
endcase
end
WRITE : begin
if ( clk_div ) begin //74HC595 serial clock has spe
ed requirements, it needs to follow the divided beat
if ( cnt_write >= 6'd33 )cnt_write <= 1'b0 ;
else cnt_write <= cnt_write + 1'b1 ;
case ( cnt_write )
//74HC595 is a serial to parallel chi
p, 3 inputs can produce 8 outputs, and can be used in cascade
//74HC595 For timing implementation, r
efer to 74HC595 chip manual
6'd0 : begin sclk_out <= LOW ; sdio_
out <= data_reg [ 15 ] ; end //SER update data at the falling edge of SCK
6'd1 : begin sclk_out <= HIGH ; end
//SCK SER data is stable at the rising edge
6'd2 : beginsclk_out <= LOW ; sdio_o
ut <= data_reg [ 14 ] ; end
6'd3 : begin sclk_out <= HIGH ; end
6'd4 : begin sclk_out <= LOW ; sdio_
out <= data_reg [ 13 ] ; end
6'd5 : begin sclk_out <= HIGH ; end
6'd6 : begin sclk_out <= LOW ;sdio_o
ut <= data_reg [ 12 ] ; end
6'd7 : begin sclk_out <= HIGH ; end
6'd8 : begin sclk_out <= LOW ; sdio_
out <= data_reg [ 11 ] ; end
6'd9 : begin sclk_out <= HIGH ; end
6'd10 : begin sclk_out <= LOW ; sdio_
out <= data_reg [10 ] ; end
6'd11 : begin sclk_out <= HIGH ; end
6'd12 : begin sclk_out <= LOW ; sdio_
out <= data_reg [ 9 ] ; end
6'd13 : begin sclk_out <= HIGH ; end
6'd14 : begin sclk_out <= LOW ; sdio_
out <= data_reg [ 8 ] ; end
6'd15: begin sclk_out <= HIGH ; end
6'd16 : begin sclk_out <= LOW ; sdio_
out <= data_reg [ 7 ] ; end
6'd17 : begin sclk_out <= HIGH ; end
6'd18 : begin sclk_out <= LOW ; sdio_
out < = data_reg [ 6 ] ; end
6'd19 : begin sclk_out <=HIGH ; end
6'd20 : begin sclk_out <= LOW ; sdio_
out <= data_reg [ 5 ] ; end
6'd21 : begin sclk_out <= HIGH ; end
6'd22 : begin sclk_out <= LOW ; sdio_
out <= data_reg [ 4 ] ; end

```

```

ut <= data_reg [ 3 ] ; end

out <= data_reg [ 2 ] ; end

ut <= data_reg [ 1 ] ; end

out <= data_reg [ 0 ] ; end

//When the 16-bit data transmission is completed, RCK is pulled high, and the output is effective
<= MAIN ; end

6'd23 : begin sclk_out <= HIGH ; end
6'd24 : begin sclk_out <= LOW ; sdio_o

6'd25 : begin sclk_out <= HIGH ; end
6'd26 : begin sclk_out <= LOW ; sdio_

6'd27 : begin sclk_out <= HIGH ; end
6'd28 : begin sclk_out <= LOW ; sdio_o

6'd29 : begin sclk_out <= HIGH ; end
6'd30 : begin sclk_out <= LOW ; sdio_

6'd31 : begin sclk_out <= HIGH ; end
6'd32 : begin rclk_out <= HIGH ; end

6'd33: begin rclk_out <= LOW ; state

default : state <= IDLE ;

endcase
end else begin
sclk_out <= sclk_out ;
sdio_out <= sdio_out ;
rclk_out <= rclk_out ;
cnt_write <= cnt_write ;
state <= state ;

end
end
default : state <=IDLE ;
endcase
end
end
endmodule

```

## ====Summary====

This section mainly explains the related principles and software design of the digital tube display. You need to master it while creating your own project, and generate the FPGA configuration file loading test through the entire design process. If you are not familiar with the use of Diamond software, please refer to here: [Use of Diamond](#) .

## ====Related Information====

Use STEP-MXO2 second generation digital control Scanner: subsequent download connection will be updated  
using the STEP-MAX10 a digital scanner: subsequent download link will be updated